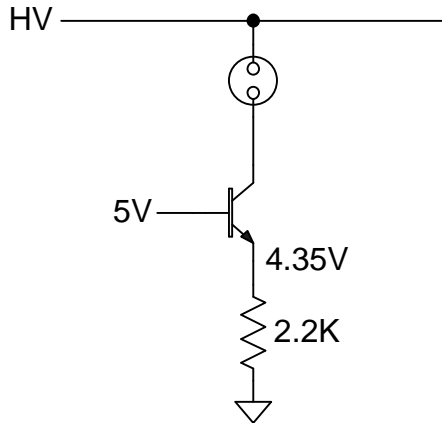


Single Transistor Current Sink



$$I = 4.35V / 2.2K = \sim 2mA$$

This circuit has a current drift over temperature because of the $-2.2mV/Deg-C$ of the V_{be} of the transistor. This can be minimized (As a percentage) by making the voltage across the setting resistor as large as possible. As shown, the typical swing would be:

$$\begin{aligned} & 25C -25/+60 \\ & = \\ & 4.35V +55/-132mV \\ & = \\ & 1.98mA -0.03/+0.05mA \end{aligned}$$

The power dissipation across the setting resistor would be $\sim 9mW$ and proportional to the duty cycle applied when dimming. There is no current overshoot since the transistor is self regulating (No reference start up) and the turn on time is the same as the transistor itself.

Since the V_{ce-sat} of even a bad NPN will be no more than a few hundred milli-volts at these currents, this sets the minimum collector voltage to about 5V, where the maximum for SOA would simply be the rated device power divided by the current: A typical SOT23 NPN is rated for 300mW so the maximum allowable V_{ce} would be 150V at 2mA!

Ripple on the power supply is automatically smoothed out by the transistor up to its corner frequency so power supply ripple such as seen by constant off time boost converts does not show up as flicker in the display.

Current from the control logic is simply the emitter current divided by the h_{fe} (beta) of the transistor and results in a decrease in the sink current but since typical beta is >100 , it can usually be ignored.