

## 7544 Group

### A-D Converter

---

#### **1. Abstract**

The following article introduces and shows an application example of converting the analog input voltage input to digital values.

#### **2. Introduction**

The explanation of this issue is applied to the following condition:  
Applicable MCU: 7544 Group

### 3. Contents

#### 3.1 Setting of A-D converter

Figure 1 shows the relevant registers setting.

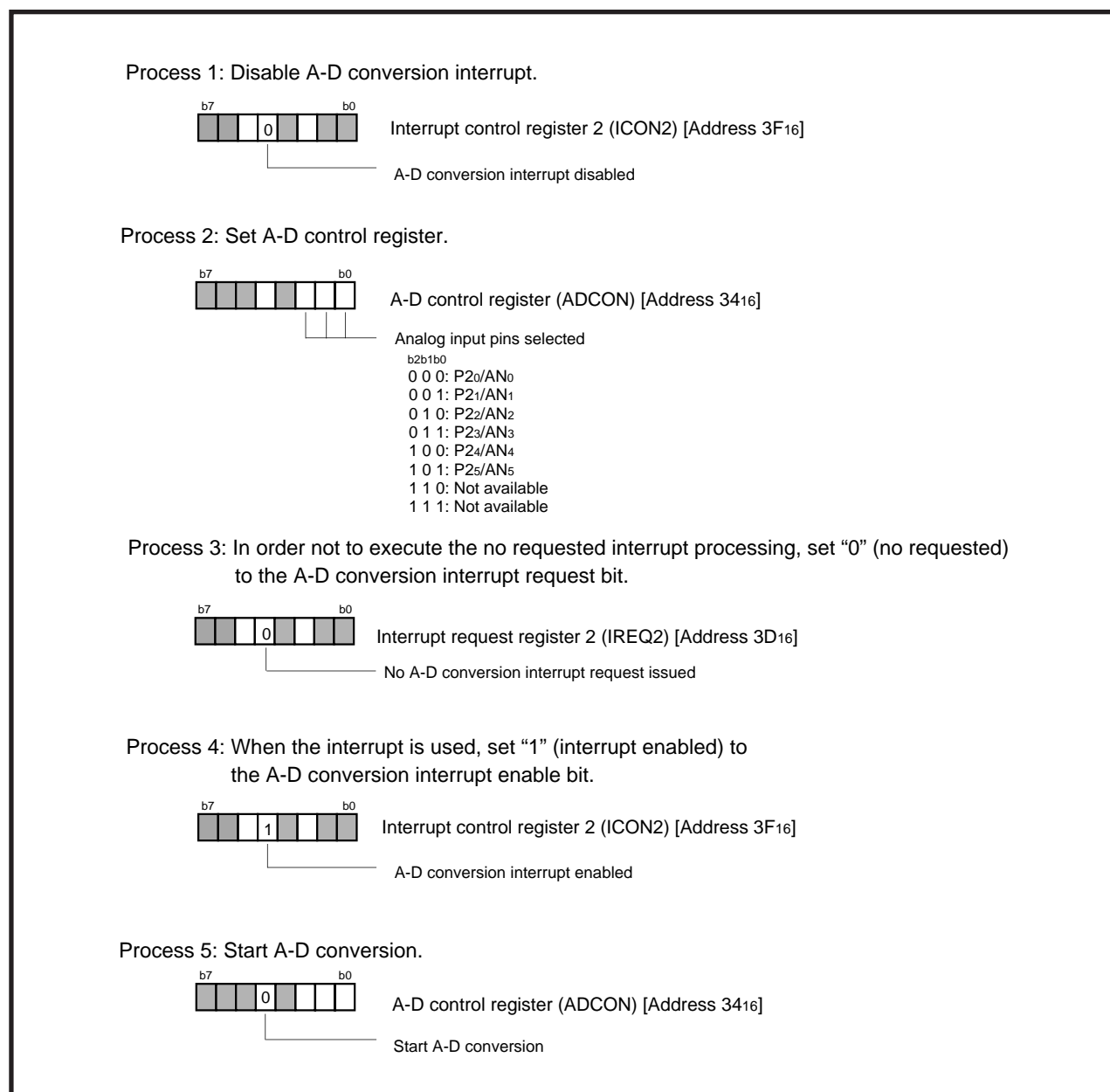


Figure 1 Relevant registers setting

### 3.2 Example of Control Procedure

**Outline:** The analog input voltage input from a sensor is converted to digital values.

**Specifications:** •The analog input voltage input from a sensor is converted to digital values.

•P20/AN0 pin is used as an analog input pin.

Figure 2 shows a connection diagram, and Figure 3 shows an example of control procedure.

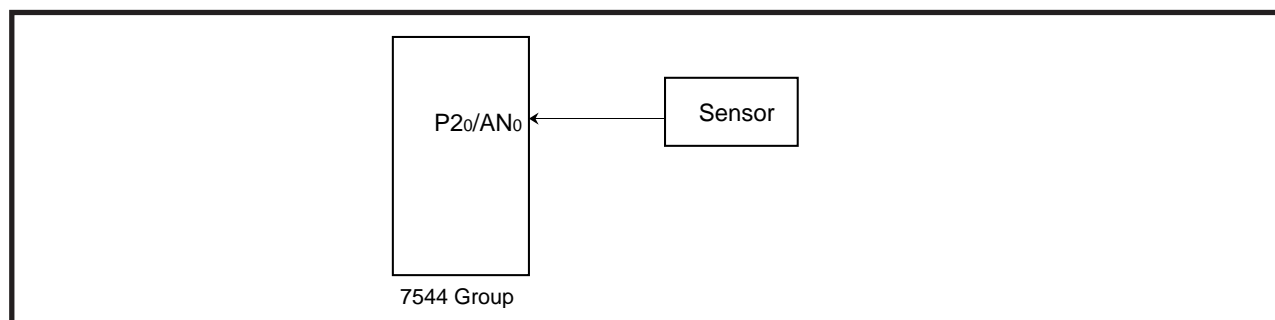


Figure 2 Connection diagram

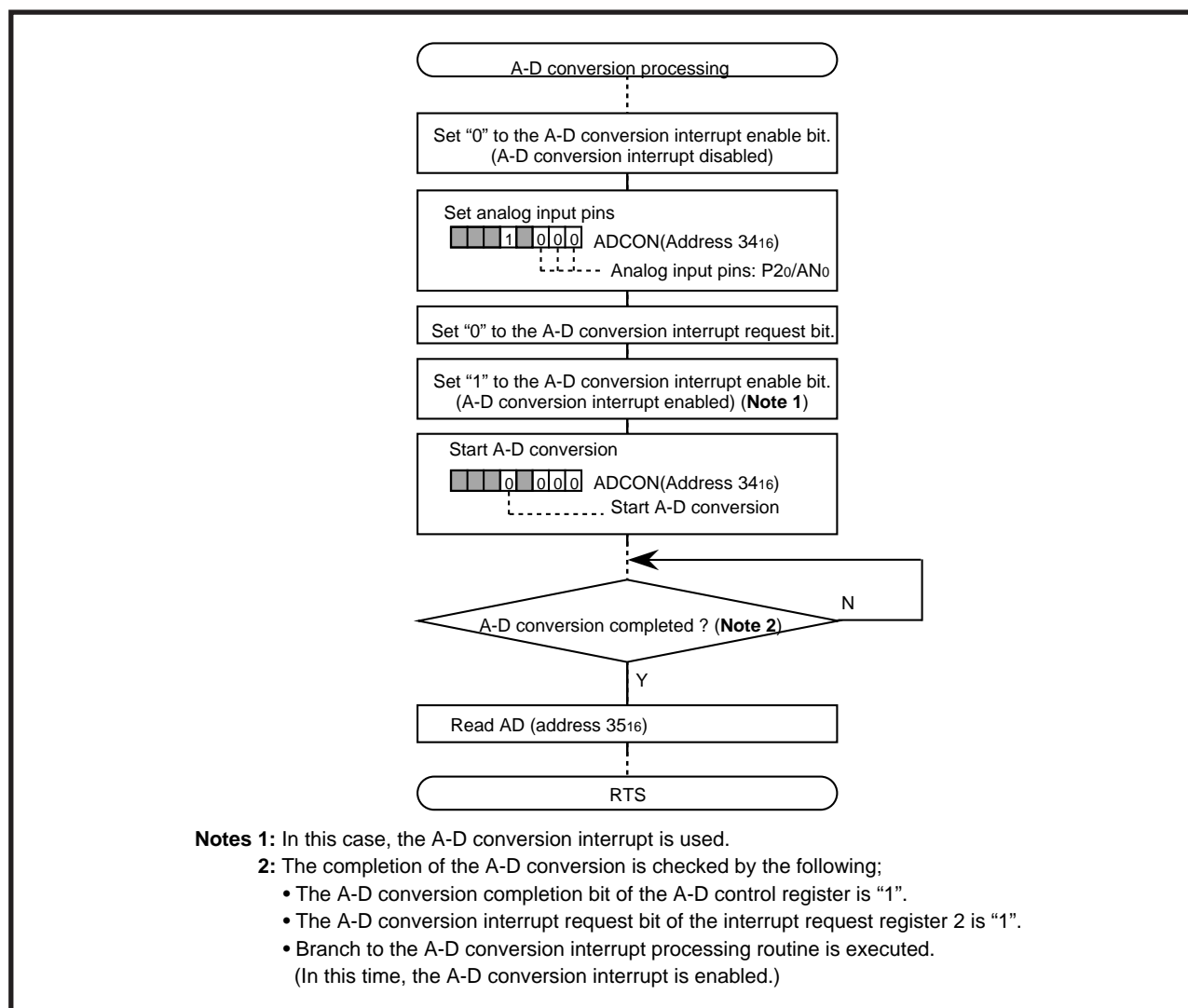


Figure 3 Control procedure

## 4. Sample Programming Code

### [Reset Start •• Main Routine Process]

```

RESET:
    SEI                      ; Interrupt disable
    CLD
    CLT
;
    LDX  #$FF                ; Set stack bottom
    TXS
;
    LDM  #%10000000,CPUM     ; Set CPU mode register
;
; Wait f(XIN) oscillation stabilizing time
;
    LDM  #%00000000,CPUM     ; Set CPU mode register
;
    LDA  #0
    LDX  #>RAM_top
RAM_clear: STA  $00,X
           INX
           BNE  RAM_clear
;
;
;-----

```

### \_\_MAIN:

```
    JSR  AD_CONVERT
```

### \_\_MAIN\_00:

```
    BRA  __MAIN
```

```
;
```

### [A-D Conversion Process]

```

AD_CONVERT:
    CLB  4,ICON2             ; disable A/D converter interrupt
    LDM  #%00010000,ADCON    ; set analog input pin (P2_0/AN0)
    CLB  4,IREQ2             ; clear A/D converter interrupt request
;
    SEB  4,ICON2             ; enable A/D converter interrupt
;                               ; (When A/D interrupt is used)
    CLB  4,ADCON             ; start A/D convert
;
AD_CONVERT_00:
    BBC  4,ADCON,AD_CONVERT_00; completed A/D convert ? -> no
    LDA  AD
    STA  Read_Data           ; read A/D convert value
    RTS
;

```

## 5. Reference

Data Sheet

7544 Group Data sheet

7544 Group Data sheet (QzROM Version)

Before using this manual, please visit our website to verify that this is the most updated document available.

Renesas Technology Corporation Semiconductor Home Page

<http://www.renesas.com/en/740>

E-mail Support

E-mail: [support\\_apl@renesas.com](mailto:support_apl@renesas.com)

REVISION HISTORY	7544 Group A-D Converter
------------------	--------------------------

Rev.	Date	Description	
		Page	Summary
1.00	Apr 01, 2003	-	First Edition issued
2.00	Nov 12, 2004	4	Sample Programming Code added.

### Keep safety first in your circuit designs!

1. Renesas Technology Corporation puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage. Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of nonflammable material or (iii) prevention against any malfunction or mishap.

### Notes regarding these materials

1. These materials are intended as a reference to assist our customers in the selection of the Renesas Technology Corporation product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Renesas Technology Corporation or a third party.
2. Renesas Technology Corporation assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.
3. All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Renesas Technology Corporation without notice due to product improvements or other reasons. It is therefore recommended that customers contact Renesas Technology Corporation or an authorized Renesas Technology Corporation product distributor for the latest product information before purchasing a product listed herein.  
The information described here may contain technical inaccuracies or typographical errors. Renesas Technology Corporation assumes no responsibility for any damage, liability, or other loss rising from these inaccuracies or errors.  
Please also pay attention to information published by Renesas Technology Corporation by various means, including the Renesas Technology Corporation Semiconductor home page (<http://www.renesas.com>).
4. When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Renesas Technology Corporation assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.
5. Renesas Technology Corporation semiconductors are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact Renesas Technology Corporation or an authorized Renesas Technology Corporation product distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical, aerospace, nuclear, or undersea repeater use.
6. The prior written approval of Renesas Technology Corporation is necessary to reprint or reproduce in whole or in part these materials.
7. If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination.  
Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.
8. Please contact Renesas Technology Corporation for further details on these materials or the products contained therein.